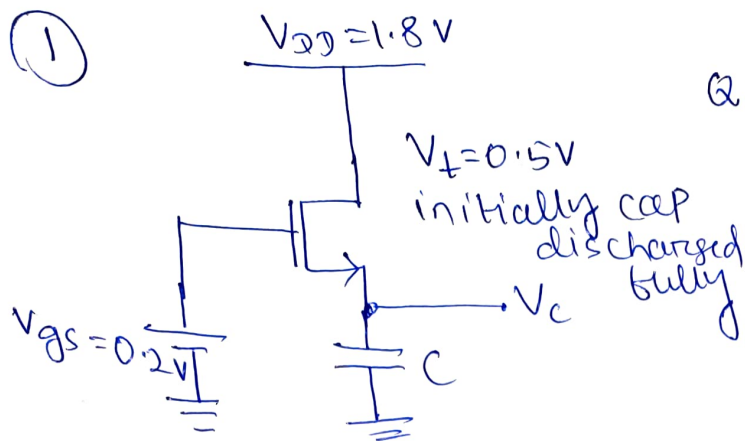



Assignment -2 :

(1)



Q: what is the value of V_c at steady state.


(2)

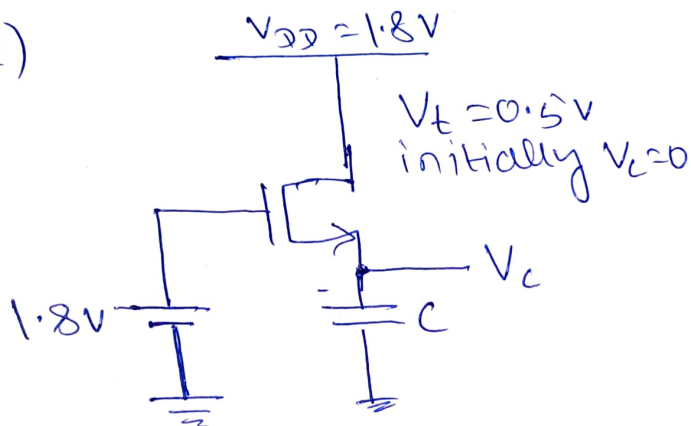

Q1: what is the value of V_c at steady state

Q2: region of operation of transistor as V_c changes.


(3)

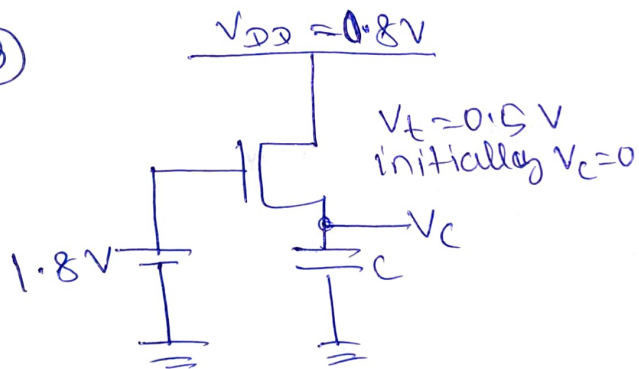

Q1: what is the value of V_c at steady state.

Q2: regions of operation of transistors as V_c changes.


(4)

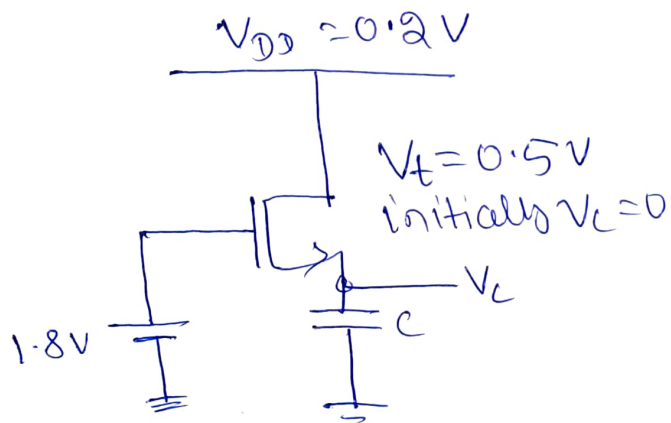

Q: what is the value of V_c at steady state.


Q: region of operation of transistor as V_c changes.

5

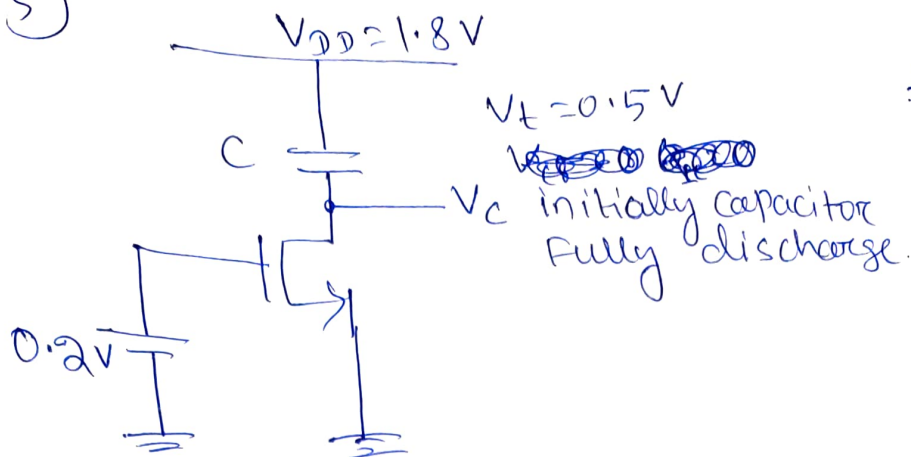


Q: what is the value of V_c at steady state

6

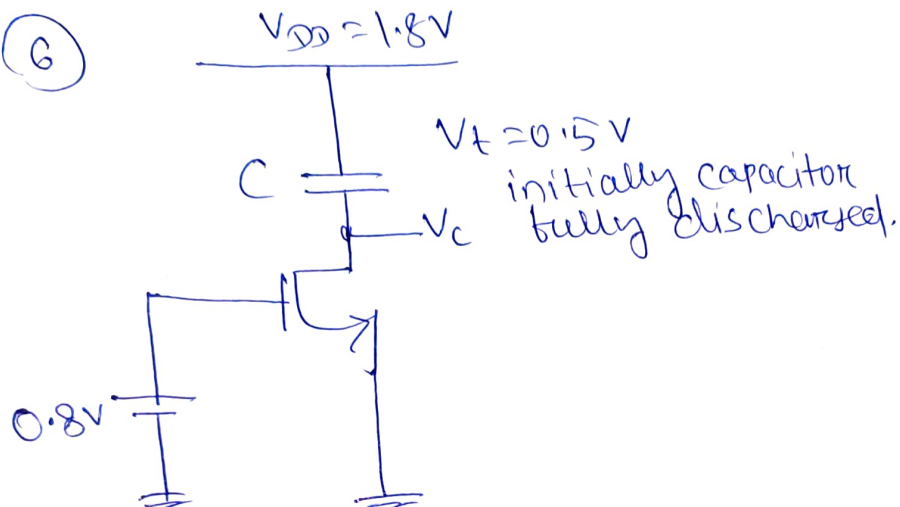

Q: what is the value of V_c at steady state.


7

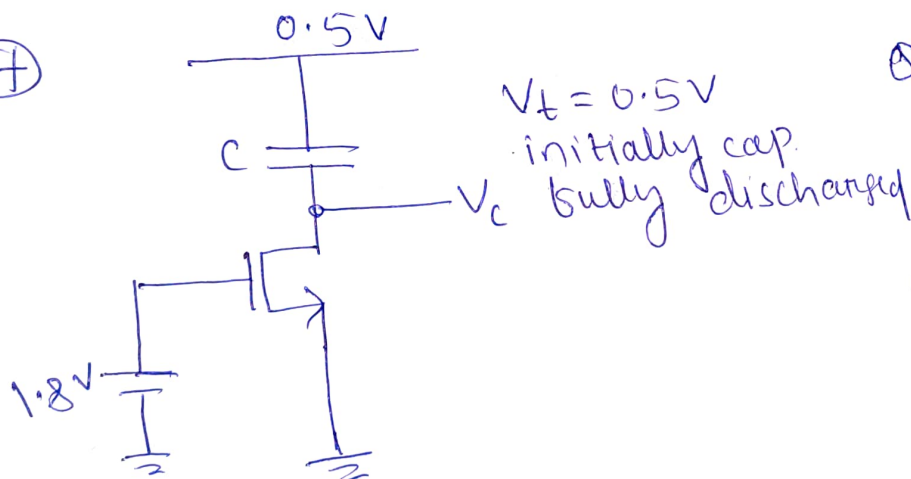






Q: what is the value of V_c at steady state.


Q: Find the region of operation.

8

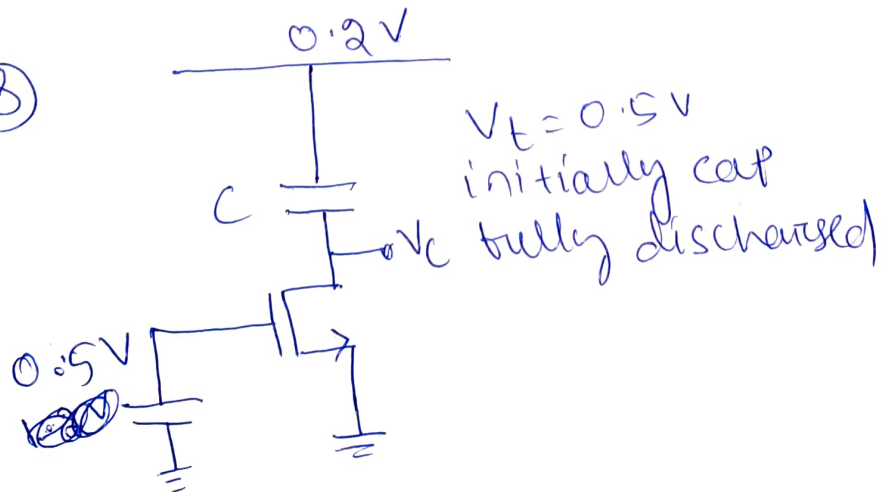


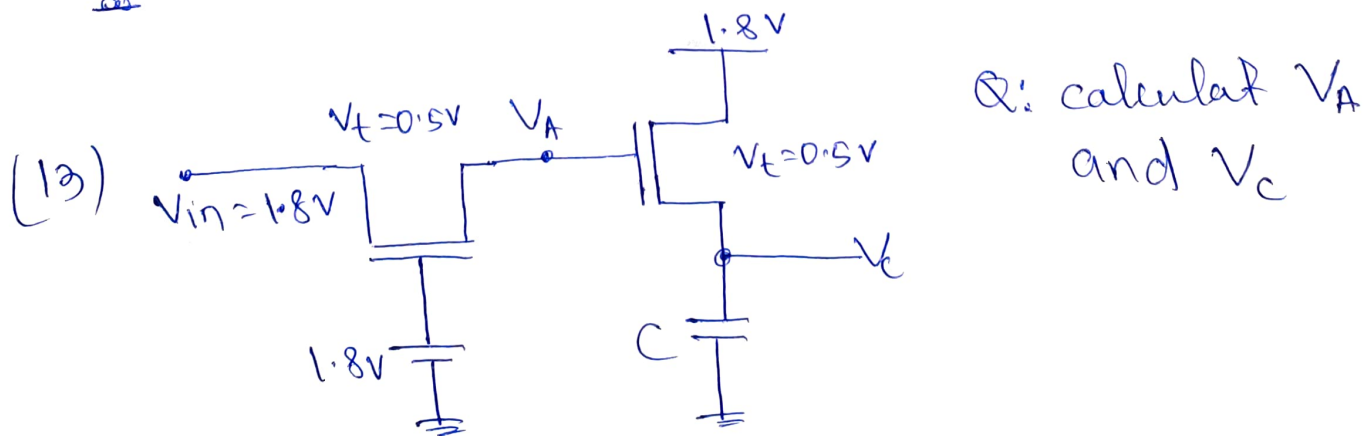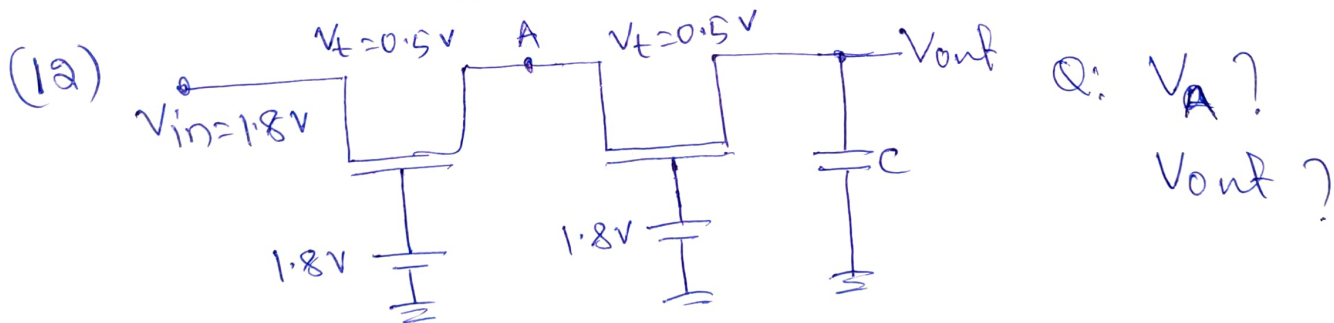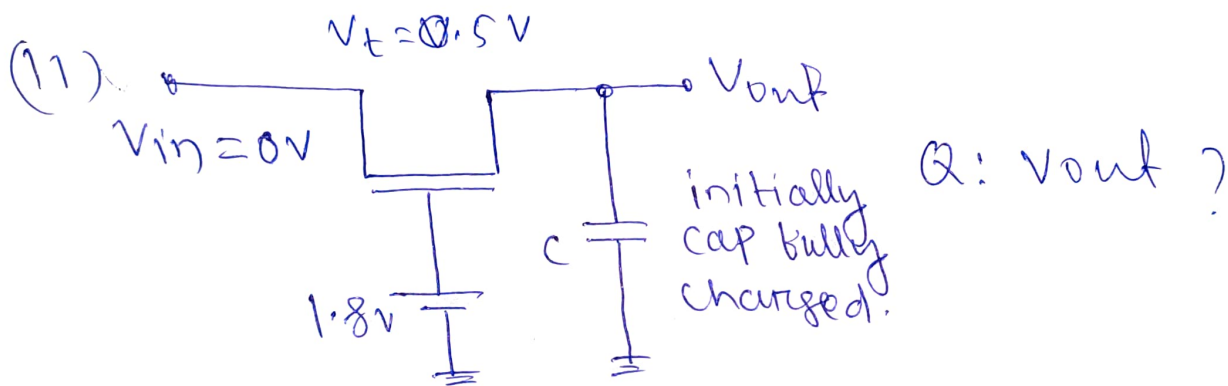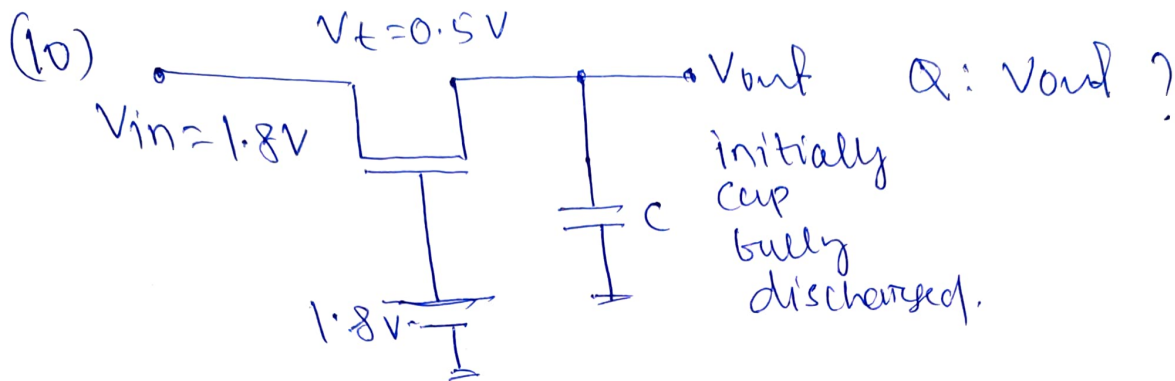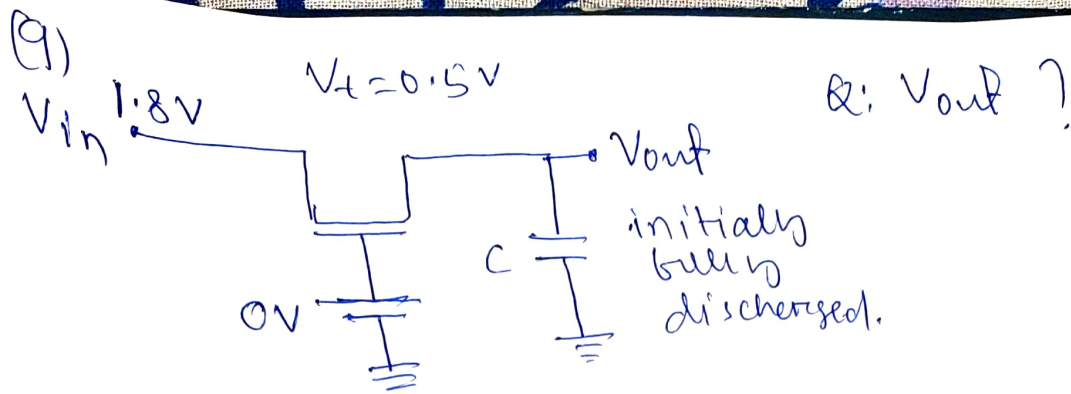Q: what is the value of V_c at steady state.




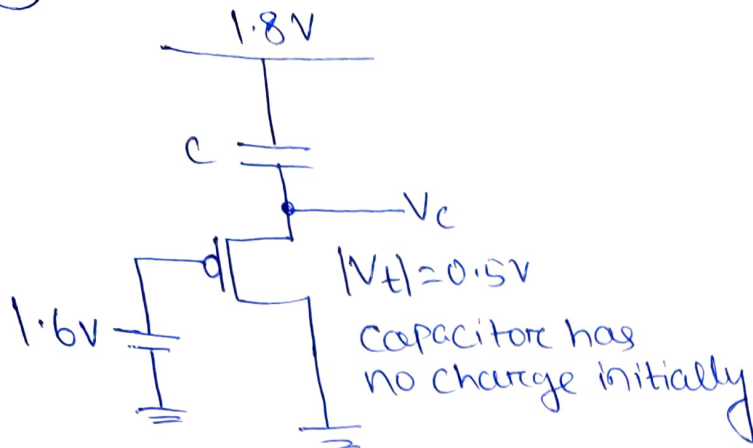

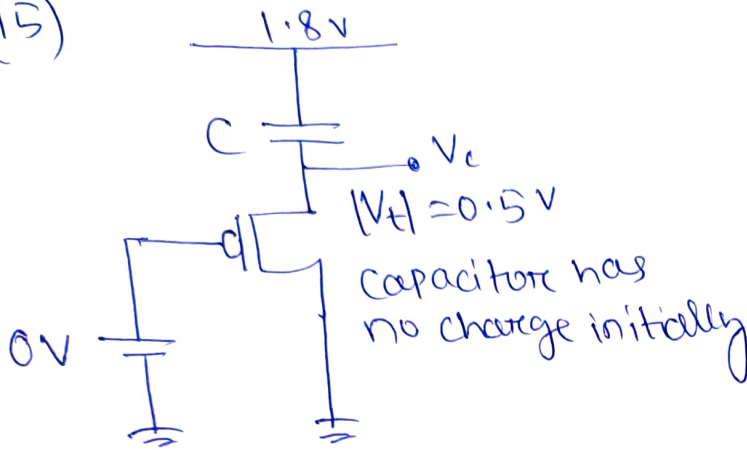
Q: calculate V_c at steady state and the region of operation of the MOSFET.



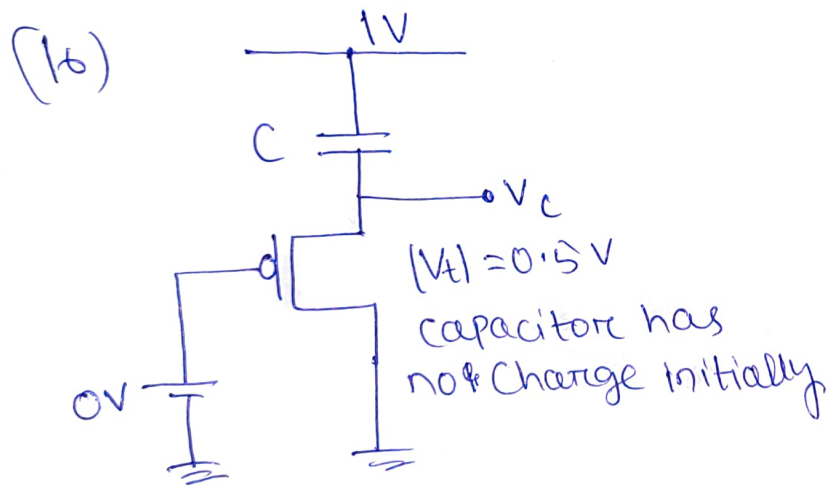
Q: calculate V_c at steady state and the region of operation of the MOSFET.



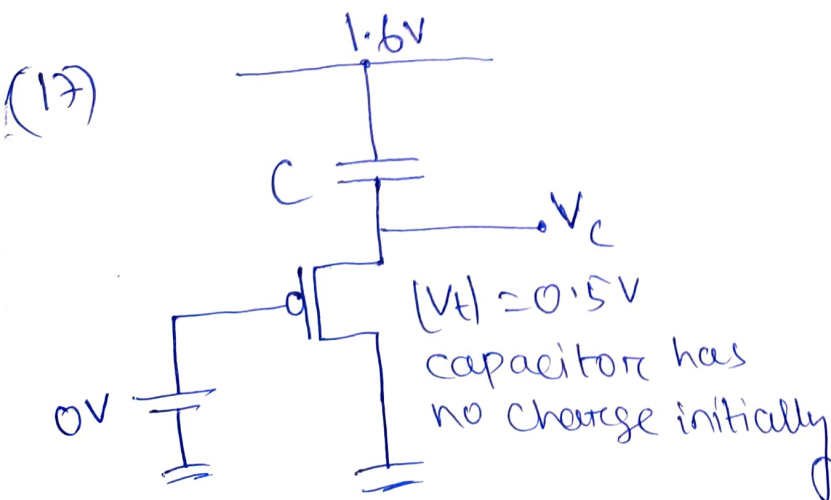
Q: calculate V_c at steady state and the region of operation of the MOSFET.



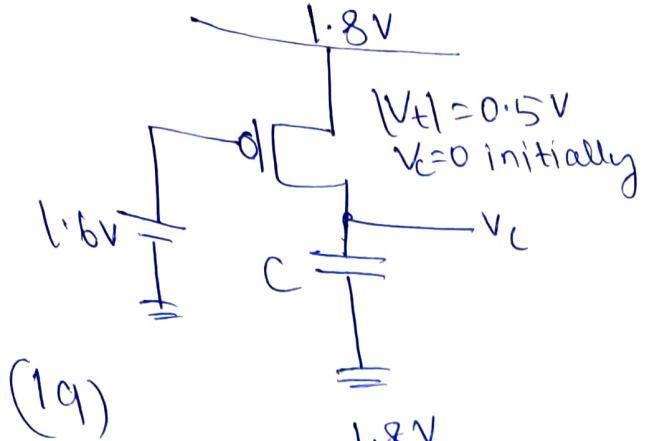
Q: calculate V_c at steady state and the region of operation of the MOSFET.



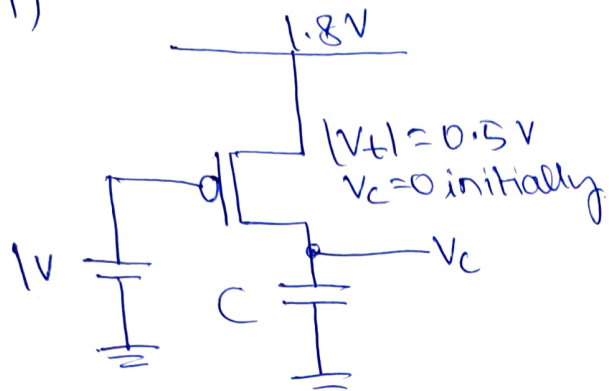
Q: calculate V_c at steady state and the region of operation of MOSFET



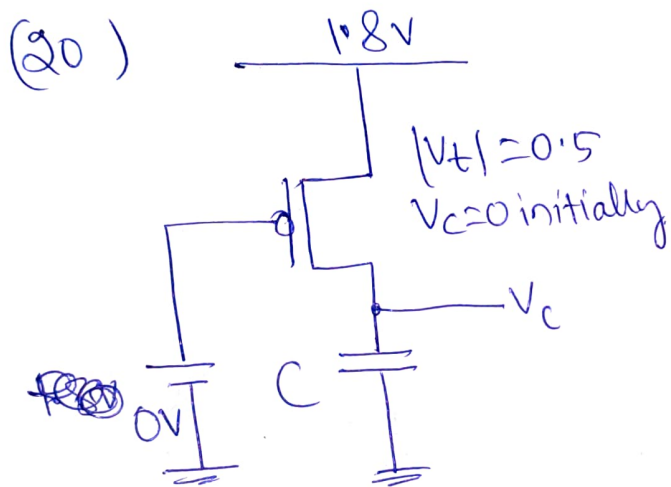Q: calculate V_c at steady state and the region of operation of MOSFET




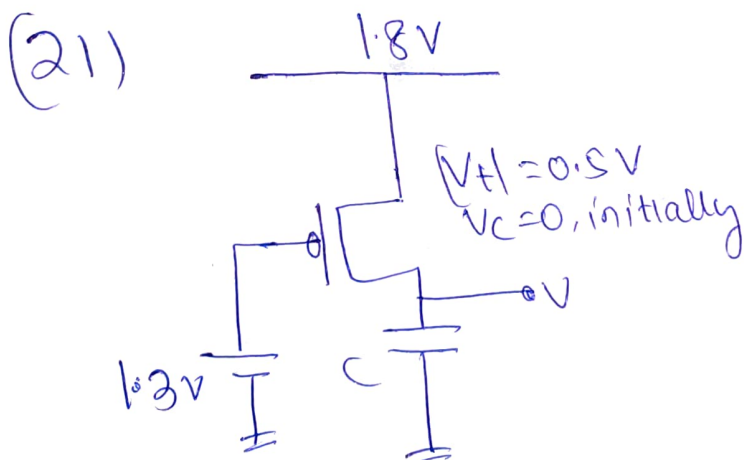Q: calculate V_c at steady state and the region of operation of MOSFET




Q: calculate V_c at steady state and the region of operation of MOSFET.

(22)

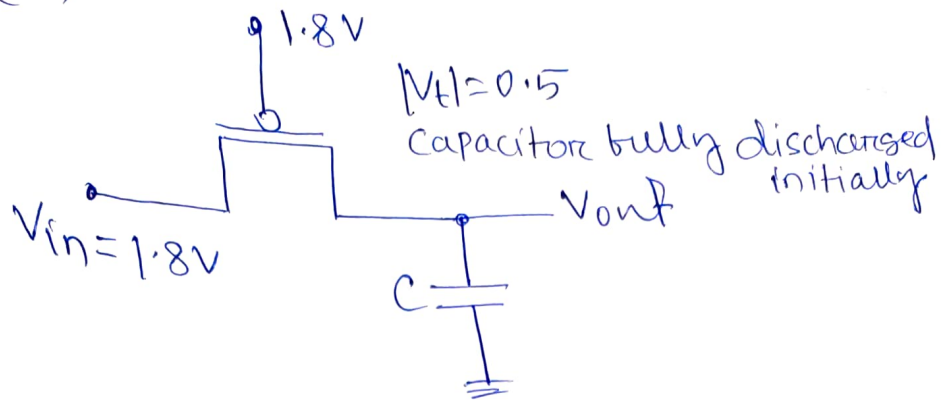


Q: calculate V_{out}

(23)

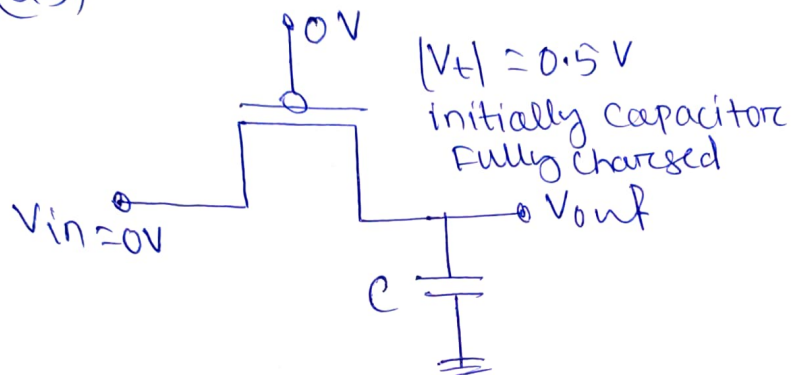


Q: calculate V_{out}

(24)

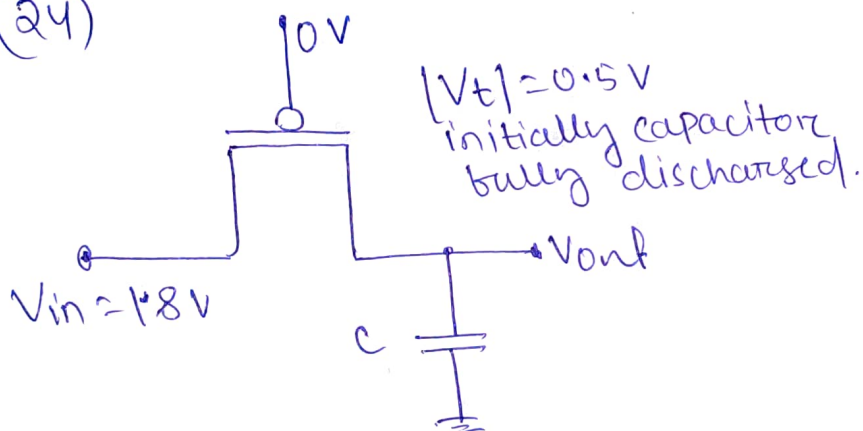


Q: calculate V_{out}

(25)

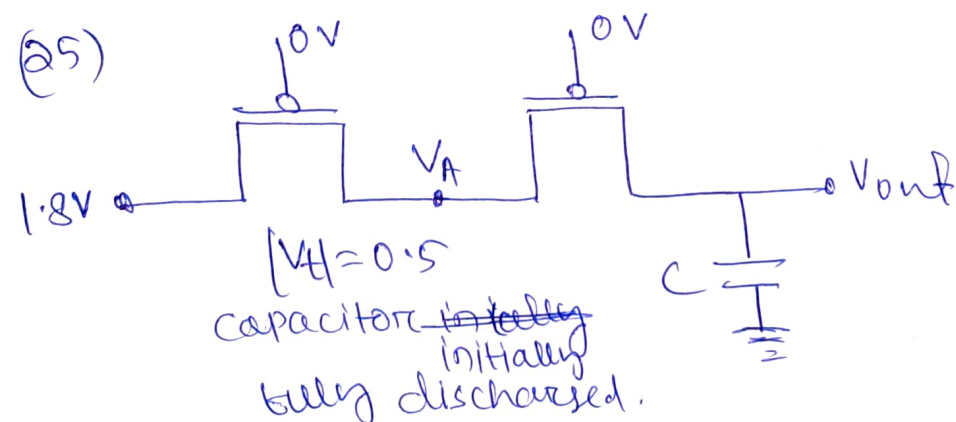


Q: calculate V_A and V_{out}

(26)

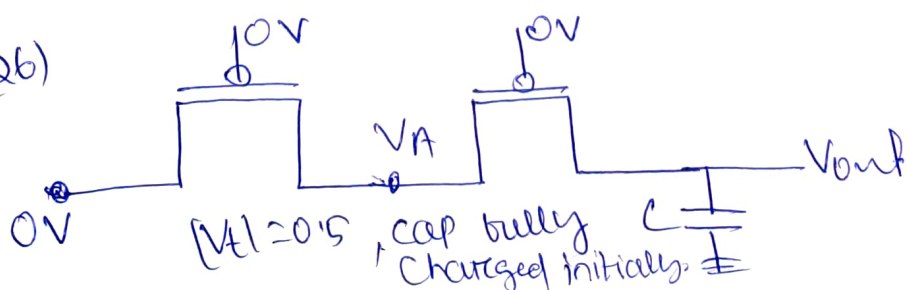

Q: calculate V_A and V_{out}

(97)

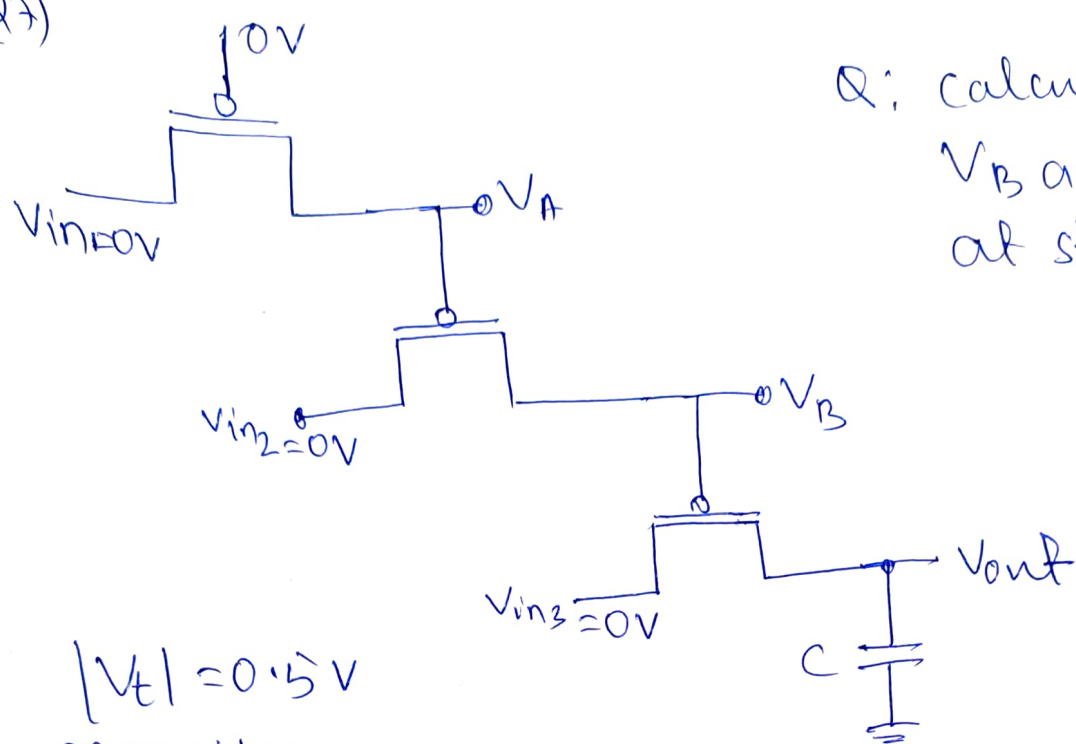

Q: calculate V_A , V_B and V_{out} at steady state.

$$|V_t| = 0.5V$$

~~capacitors~~

all node capacitors are
fully charged initially.

$V_{out} = 1.8V$ Initially