
 


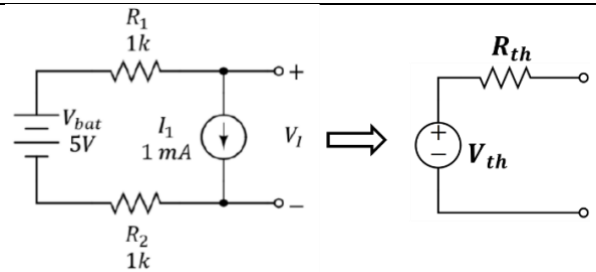Question-1
The voltage across current source I_1 (V_I) is:




Question-2
The Thevenin equivalent (V_{th} , R_{th}) of the network:




Question-3
Two capacitors of value C and $2C$, are charged to 1V and 2V respectively and then connected in parallel with same polarity. The voltage across the parallel capacitors is:

 Question-4
 $1\mu s$ after a step input of 1V, the output voltage V_{OUT} is ($1/e=0.368$):



 
Question-5

Forward bias voltage of the diode is 0.7V. The current in the circuit is:



 Question-6


At very high frequencies the peak output voltage V_o :



Question-7


The circuit shown is a filter of type:

_____ with $f_{3dB} =$ _____ rad/sec

 

 
Question-8

Using principle of superposition, the expression for V_{out} is:




 
Question-9

In the circuit shown, D1, D2, D3 are identical, and inputs E1, E2 and E3 are '0' V for logic '0' and '10' V for logic '1' what logic gate does the circuit represents:



  Question-10

The state-diagram shown for the logic circuit is:




Question-11

The state-diagram in Question-10 is a:

- (a) Moore Machine
- (b) Mealy Machine
- (c) Moore-Mealy Machine
- (d) None of the above

 
Question-12

A 2:1 MUX is connected as shown in figure. The resultant logic gate is a:




 
Question-13

A D-FlipFlop (DFF) has an inherent setup time of 0.5ns and when a delay on 0.25ns is added in the clock path, the resultant setup time is:



  
Question-14

For the circuit shown, find out v_D , when $V^+ = 10 + 1 \cos(2\pi \cdot 60 \cdot t)$ V



 
Question-15

For the circuit shown in the figure find out the output voltage, voltage across the resistor R and current through the zener diode.



 
Question-16

Calculate the node voltages and currents in the circuit assuming $\beta = 100$.



 
Question-17

For the circuit in the enhancement type NMOS threshold voltage $V_T=2V$, find the region of operation for V_D of 0.5V, 1V and 5V.



 Question-18

The switch in the circuit has been closed for a long time and it is opened at $t=0$. Find $v(t)$ for $t \geq 0$.



Question-19

What is the logic function implemented by the CMOS transistor network.

